

# The ATLAS Fast Tuner Design

Gary P. Zinkann

# Fast Tuner Development Participants


- Ken Shepard
  - Gene Clifft
  - John Bogaty
  - Gary Zinkann
  - Segey Sharamentov
  - Nemitalla Added
  - P.N.Prakash
- 
- Argonne National Lab
- Department de Fisica Nuclear, Universidade de Sao Paulo, Brasil
- Nuclear Science Center, New Delhi

# ATLAS


## Argonne Tandem Linac Accelerator System


- Medium energy heavy-ion accelerator
  - Elements from  $A = 1$  to  $A = 238$
  - Energy range variable up to  $\sim 10$  MeV/A
- Comprised of superconducting split-ring and interdigital accelerating cavities
- Cavity frequencies range from 48.5 MHz to 97 MHz
- Typical operation of 6000 hours beam on target per year
- DOE national user facility

# ATLAS BEAMS FY2000

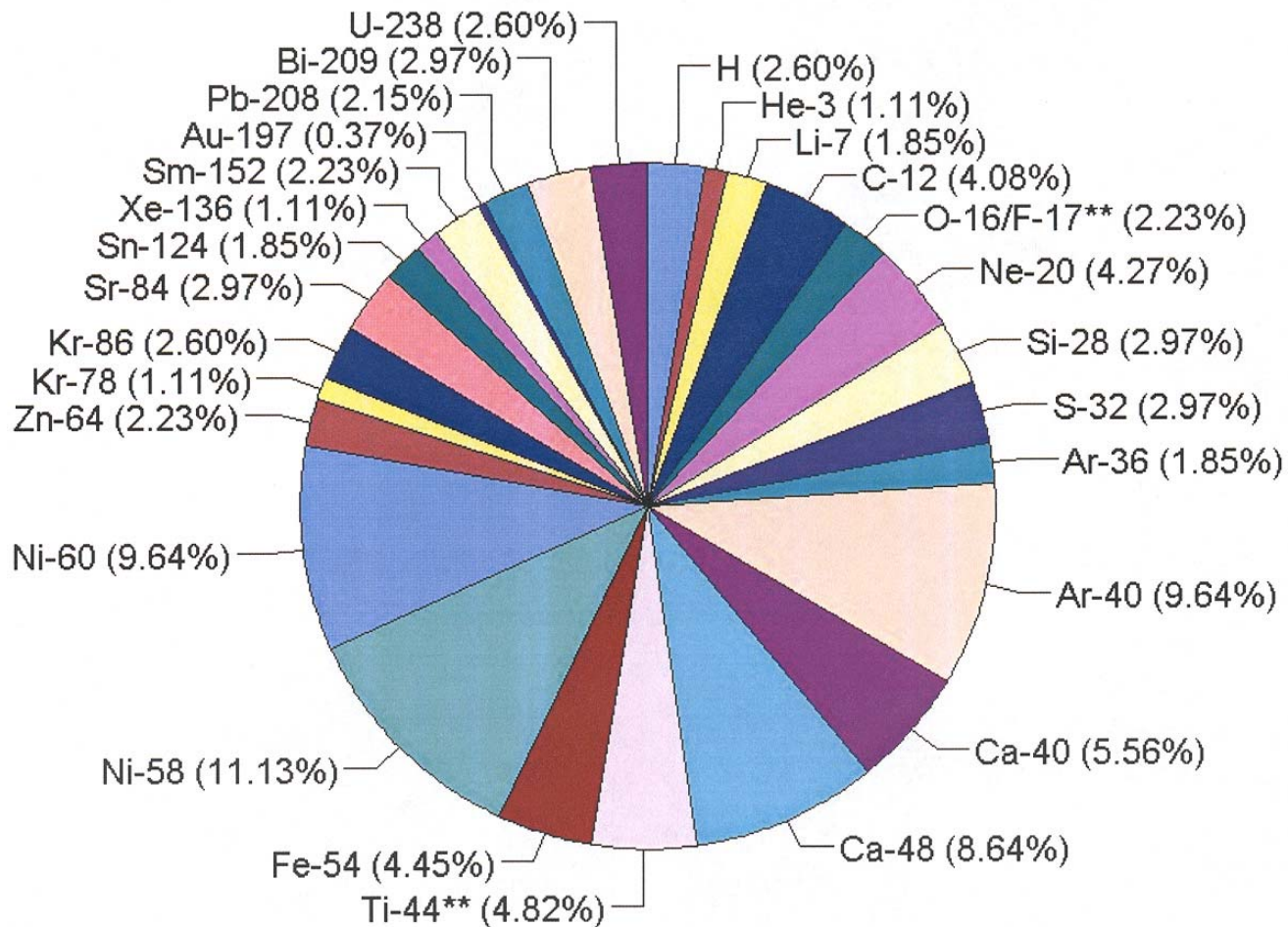

# ATLAS

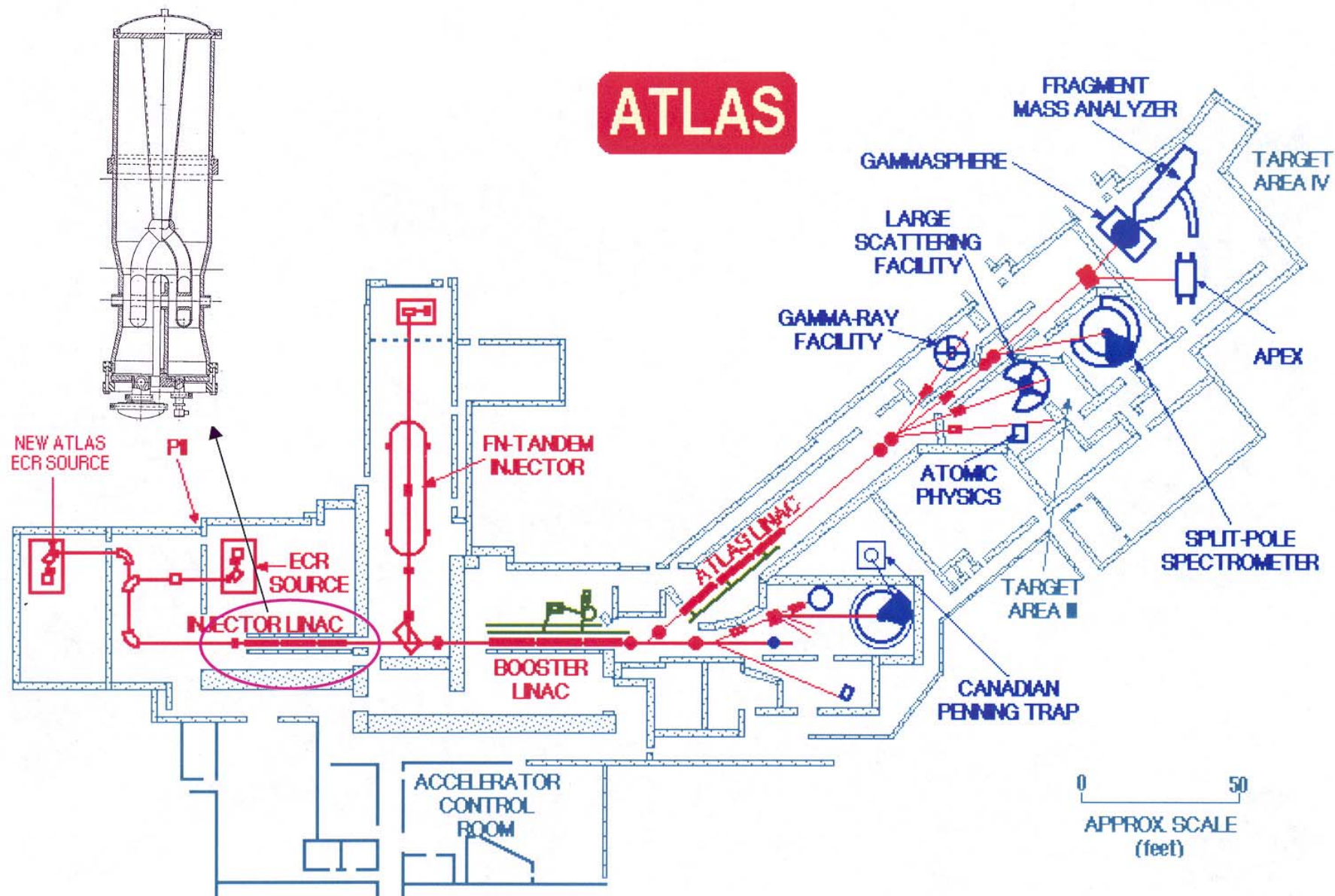


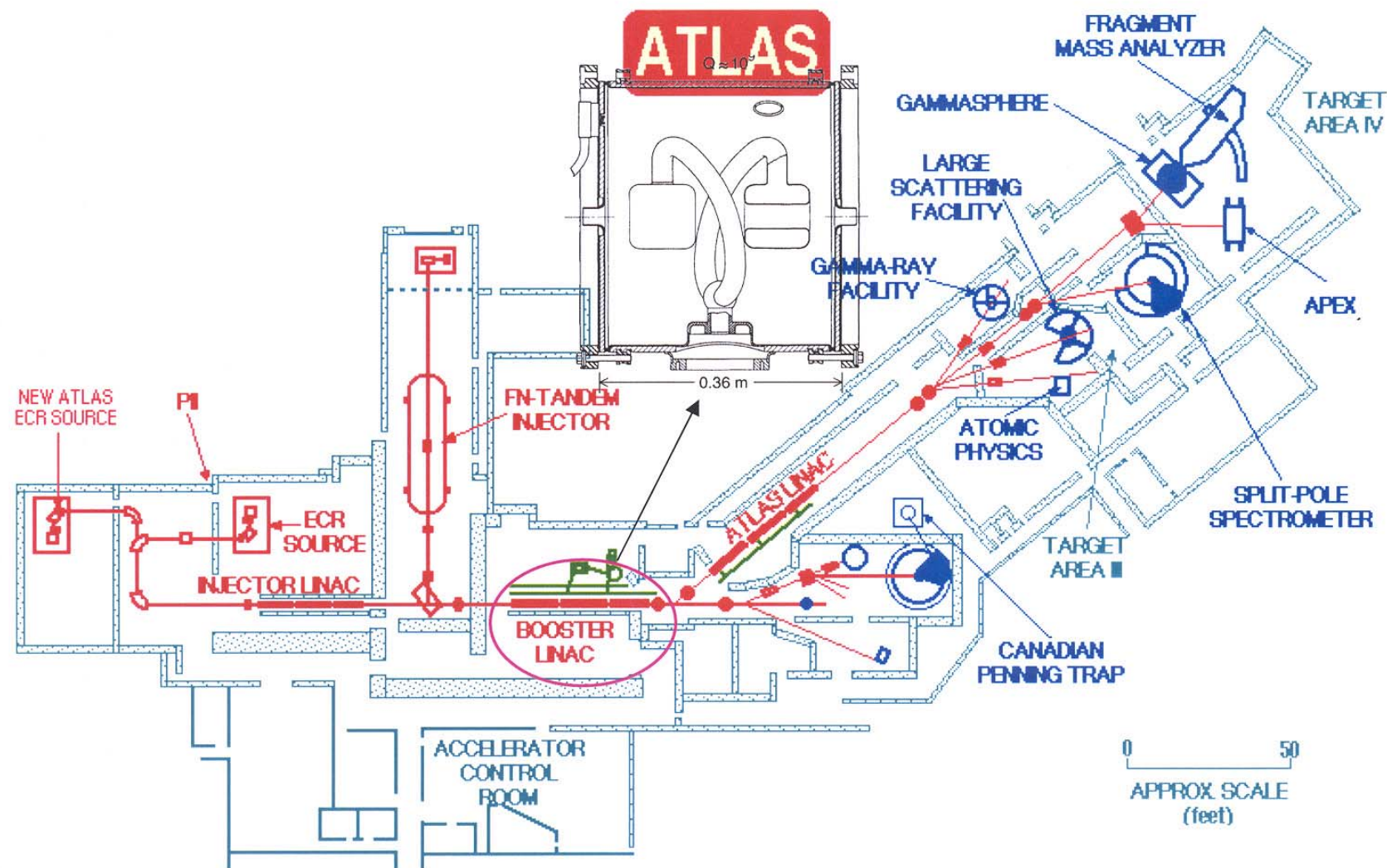

# Fast Tuner Description


- The fast tuner's function is to electronically cancel the effects of mechanical vibration on the eigen frequency and control of the RF phase with respect to a master oscillator.
- The system consists of three separate components:
  1. 77K PIN Diode Unit
  2. PIN Diode Drive Module
  3. A section of the RF Control Module
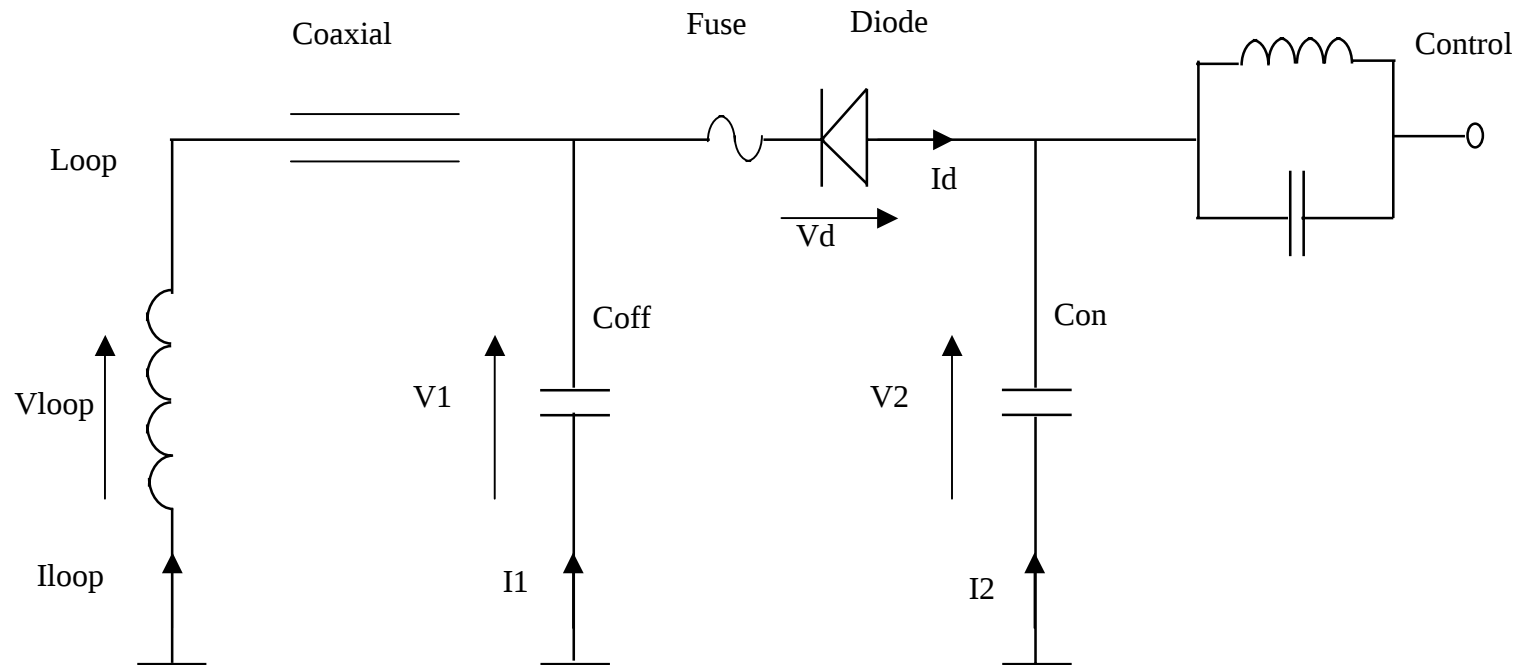
# *Simplified Equivalent Diagram of Fast Tuner*



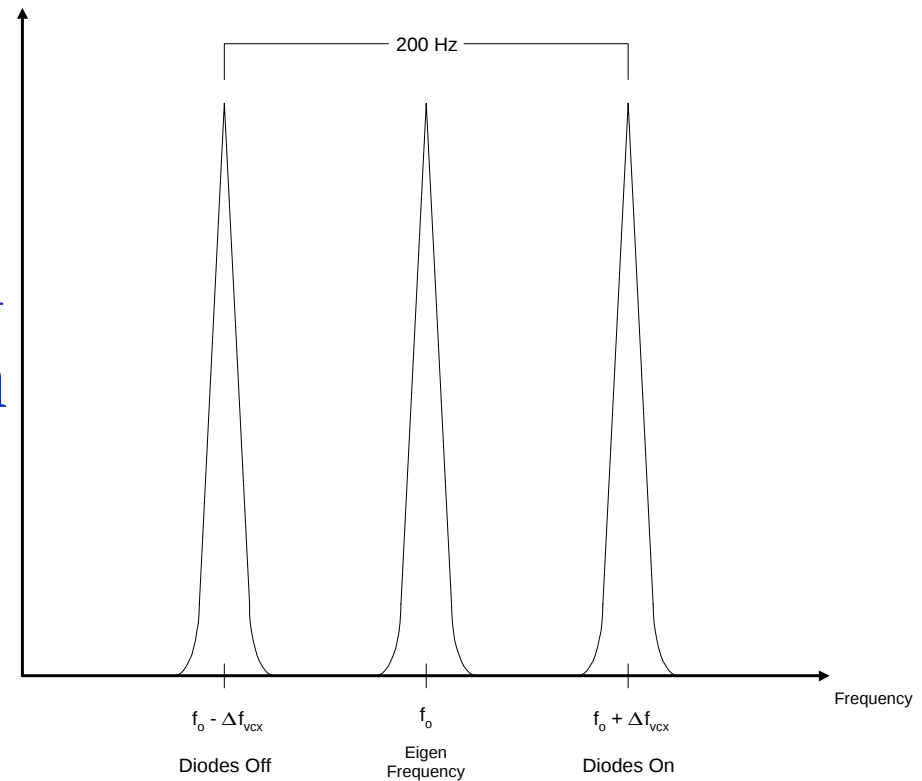
# 77 K PIN Diode Unit


- When the diodes are switched between the on and off states, the eigen frequency shifts typically 200 Hz.




# PIN Diode Switching Waveform

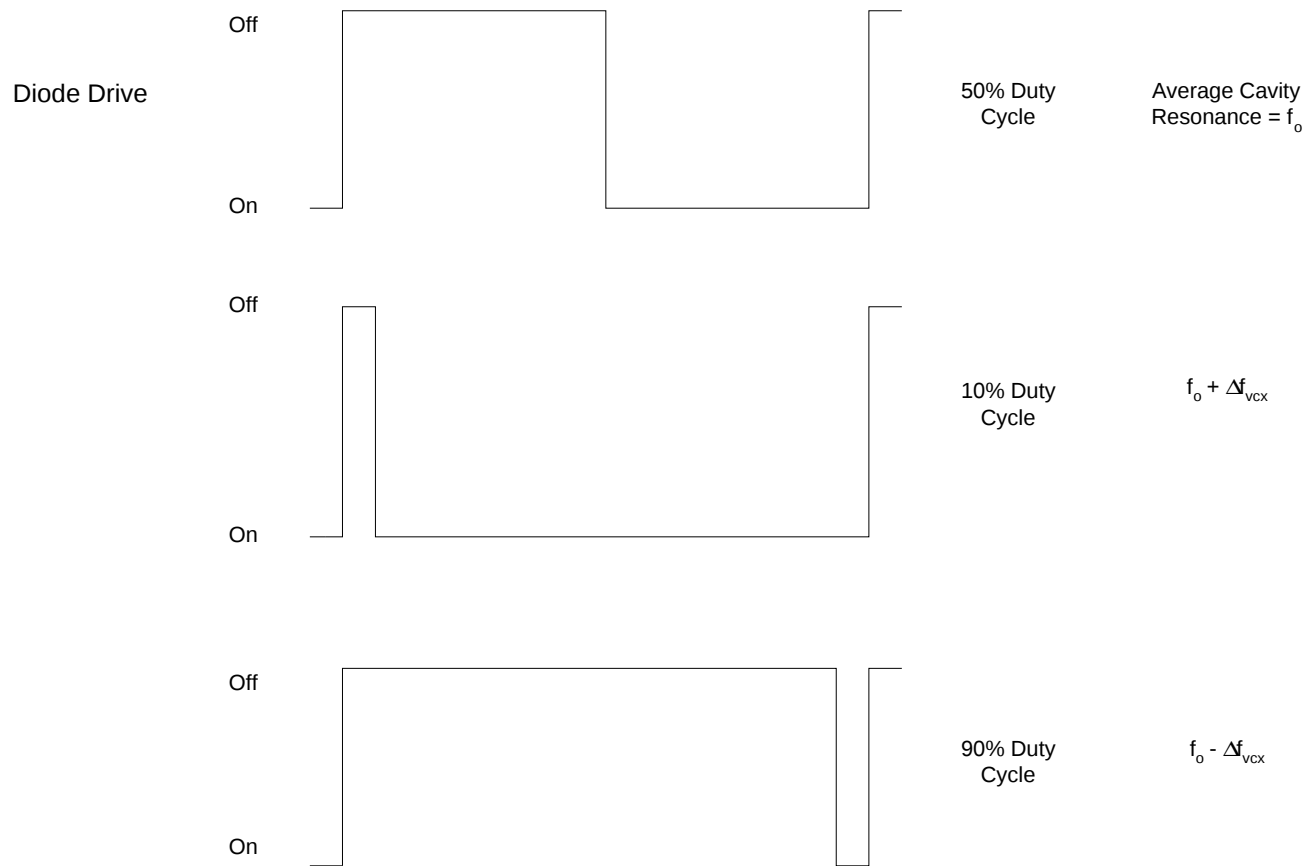


# Phase Control

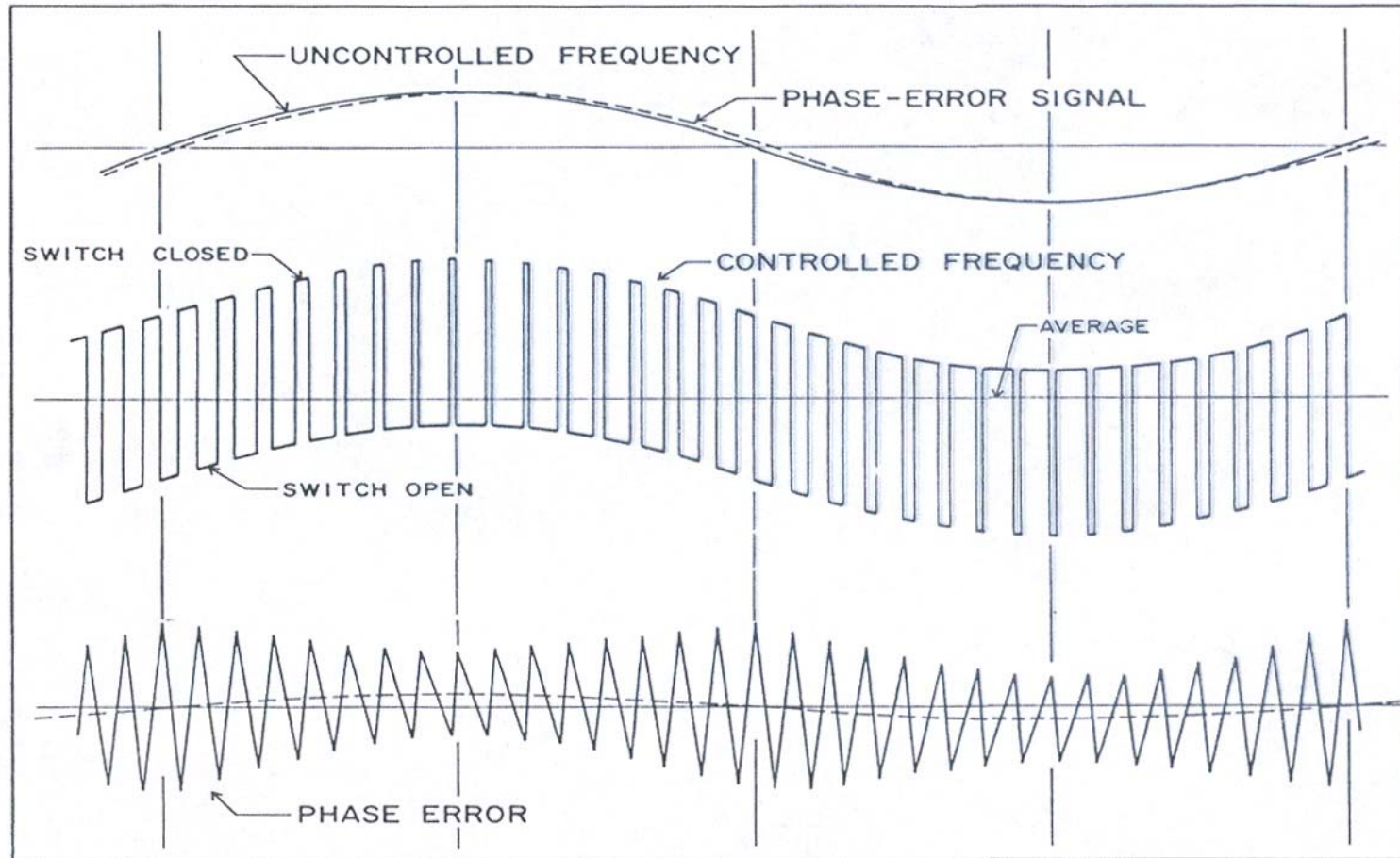
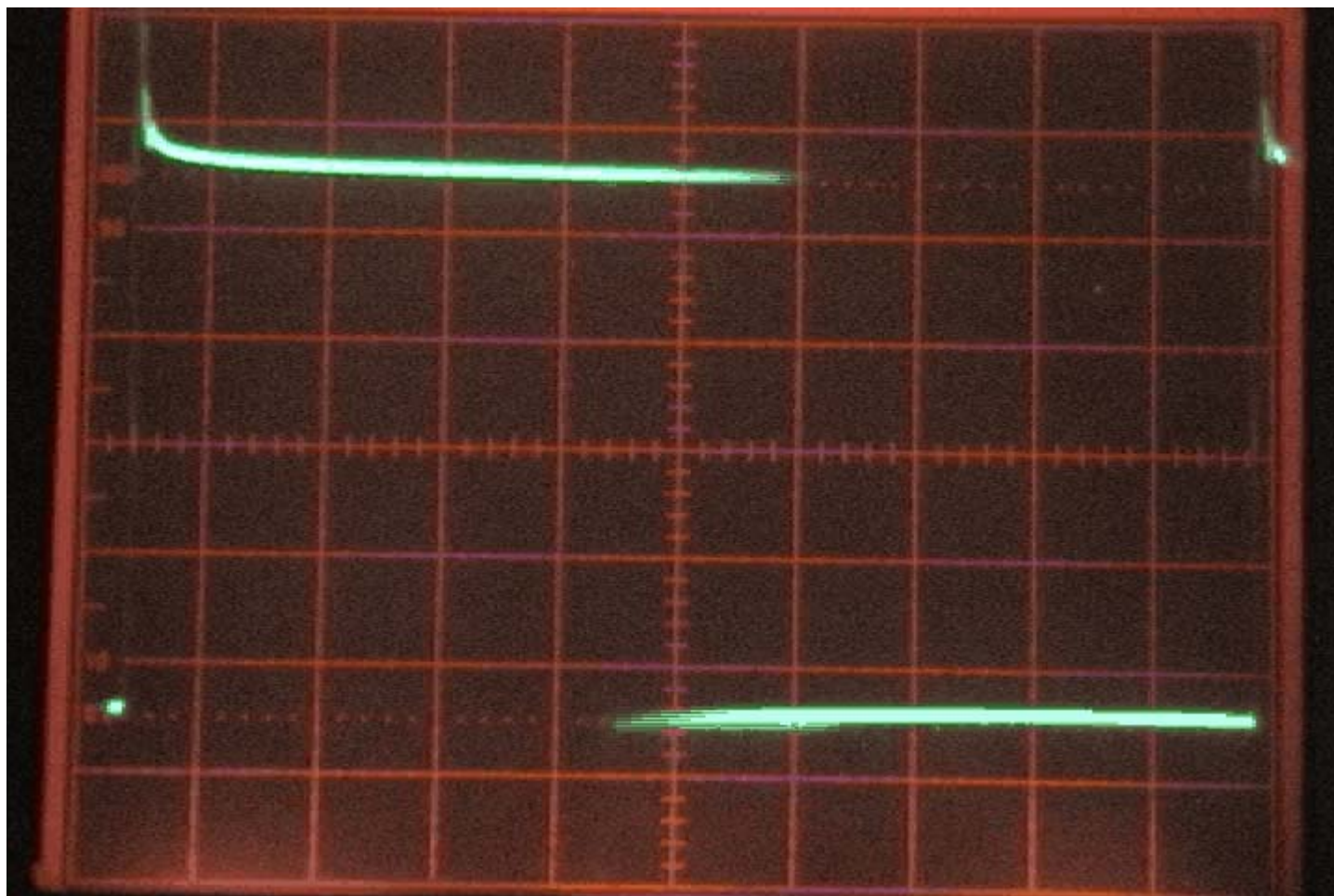
$$\theta_{\text{rad}} = 2\pi (\delta f_{\text{vcx}}) (1/2 \text{ switching period})$$



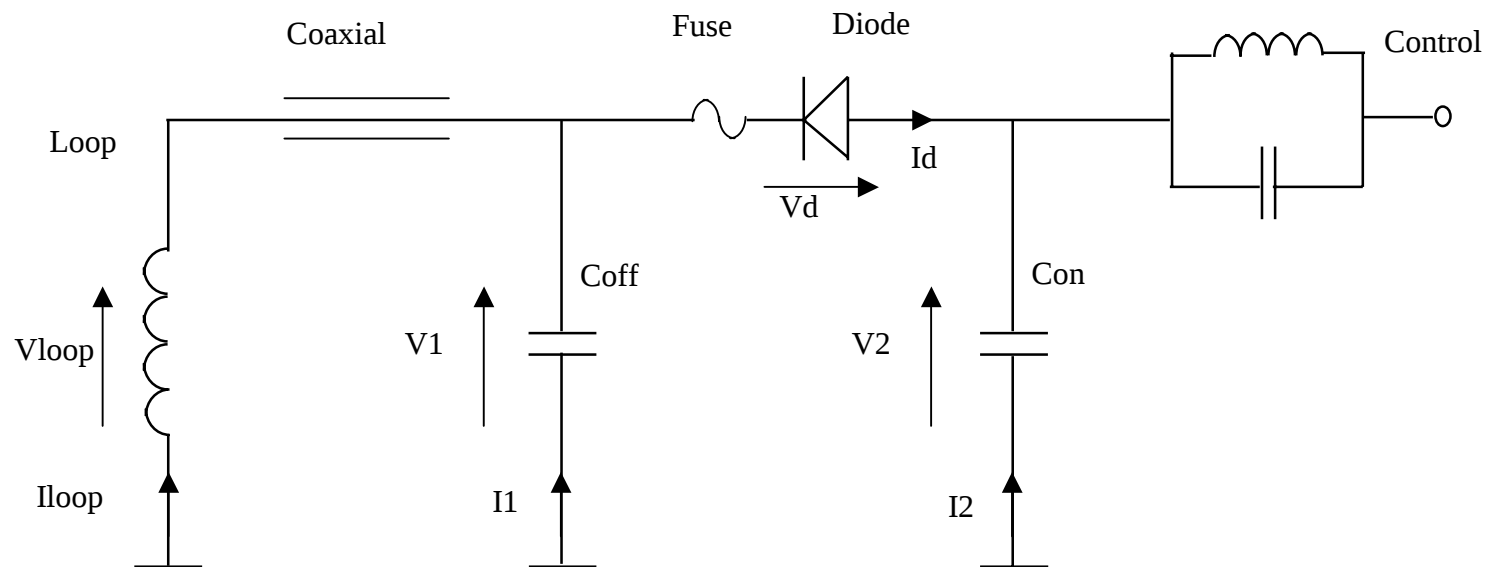
# *Simplified Equivalent Diagram of Fast Tuner*



# Nodal Schematic

LOOP VCX NOVA NODAL DIAGRAM

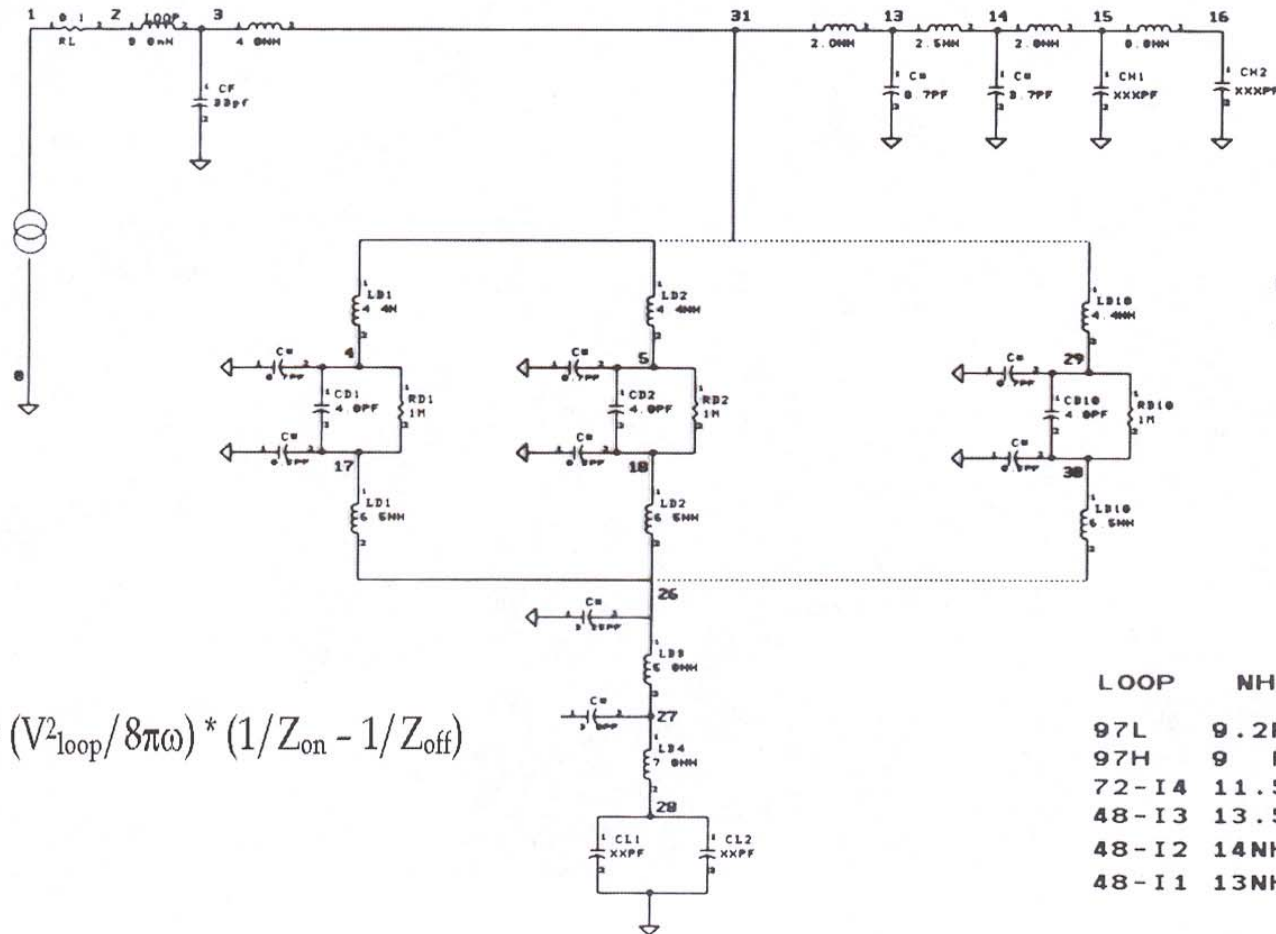


| FREQ | CH     | CL  |
|------|--------|-----|
| 97F  | 11.    | 166 |
| I1A  | 166.83 | 455 |
| I2A  | 83.83  | 455 |
| I3   | 34.34  | 505 |
| I4   | 40.40  | 192 |

| LOOP  | NH     | VOLTS        |
|-------|--------|--------------|
| 97L   | 9.2NH  | 41.4 0.080j  |
| 97H   | 9 NH   | 60.0 0.159j  |
| 72-I4 | 11.5NH | 45.0 0.141j  |
| 48-I3 | 13.5NH | 61.0 0.185j  |
| 48-I2 | 14NH   | 38.8 0.1026j |
| 48-I1 | 13NH   | 25.8 0.0367j |

$$\Delta f = (V_{loop}^2 / 8\pi\omega) * (1/Z_{on} - 1/Z_{off})$$

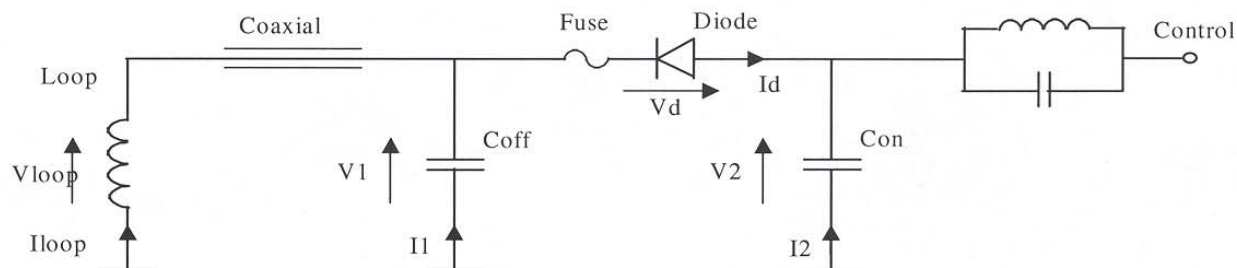*Simplified Equivalent Diagram of Fast Tuner*




*Example of 97H Resonator. Vloop = 60V Peak @ 1MV/m, Stored Energy W=0.159J.*

| Iloop,A                                 | Ploop react.,W | Ploop act.,W | Vd,V                                                         | Id,A | Pd react.,W | Pd act.,W | V1,V                       | I1,A | V2,V                        | I2,A | State        |
|-----------------------------------------|----------------|--------------|--------------------------------------------------------------|------|-------------|-----------|----------------------------|------|-----------------------------|------|--------------|
| 9.4                                     | 564            | 5.1          | 6.25                                                         | 9.4  | 58          | 0.44      | 16.6                       | 0.19 | 89.4                        | 9.3  | On<br>1MV/m  |
| 5.8                                     | 347            | 1.9          | 95.9                                                         | 2.9  | 275         | 0         | 105.2                      | 1.1  | 23.1                        | 2.4  | Off<br>1MV/m |
| Reactive Switching Power <b>14576 W</b> |                |              | Reverse Voltage <b>384 V</b><br>Reactive Power <b>4400 W</b> |      |             |           | React. Power <b>1852 W</b> |      | React. Power <b>13303 W</b> |      | Max<br>4MV/m |

$$Z_{on} = 0.11 + j6.16 \quad Z_{off} = 0.1 - j10.65 \quad \delta F = \frac{V_{loop}^2}{8\pi W} \left[ \frac{1}{\text{Im } Z_{on}} - \frac{1}{\text{Im } Z_{off}} \right] = 230.6 \text{ Hz}$$
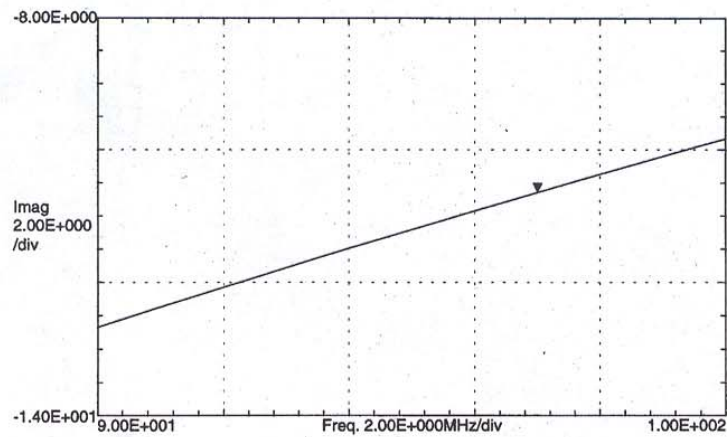
$$\text{Reactive Switching Power } P_{react} = 8\pi\delta F W E^2 = V_{loop}^2 E^2 \left[ \frac{1}{\text{Im } Z_{on}} - \frac{1}{\text{Im } Z_{off}} \right] = 14746 \text{ W.}$$




## OFF Impedance

Source Simulation

$$Z_0 = 50.0 \text{ Ohms}$$

$$Z_s = 50.0 + j 0.00 \text{ ohms}$$

$$Z_{in} = 0.1029 - j 10.646$$

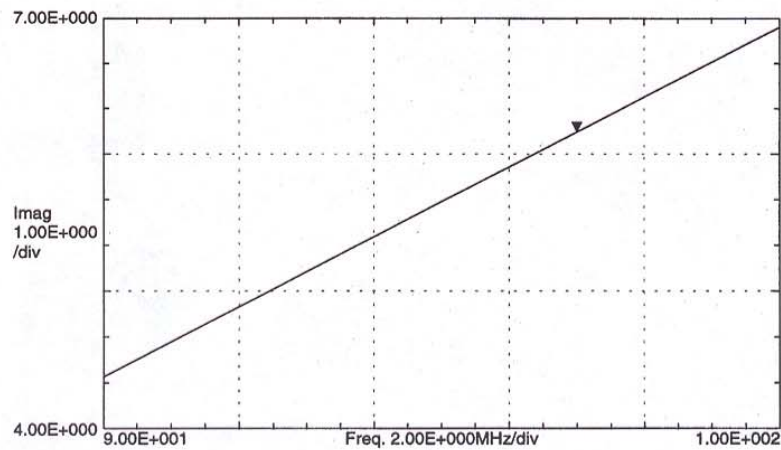

## ON Impedance


Source Simulation

$$Z_0 = 50.0 \text{ Ohms}$$

$$Z_s = 50.0 + j 0.00 \text{ ohms}$$

$$Z_{in} = 0.1097 + j 6.1604$$
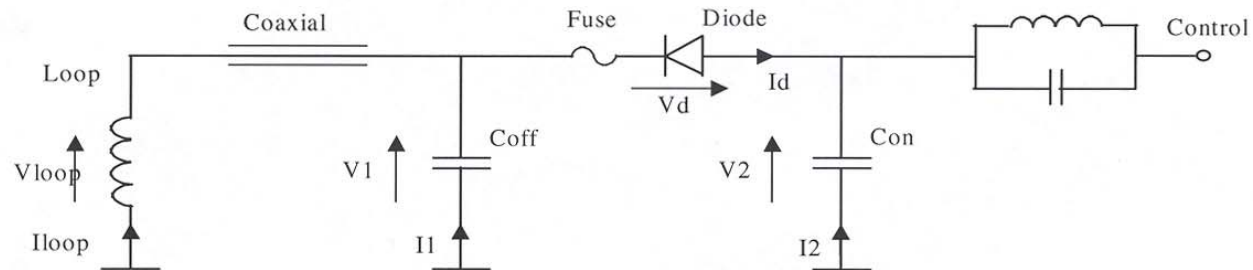
# Simplified Equivalent Diagram of Fast Tuner




Example of 97H Resonator.  $V_{loop} = 60V$  Peak @  $1MV/m$ , Stored Energy  $W=0.159J$ .

| Iloop,A                                 | Ploop react.,W | Ploop act.,W | Vd,V                                                         | Id,A | Pd react.,W | Pd act.,W | V1,V                       | I1,A | V2,V                        | I2,A | State        |
|-----------------------------------------|----------------|--------------|--------------------------------------------------------------|------|-------------|-----------|----------------------------|------|-----------------------------|------|--------------|
| 9.4                                     | 564            | 5.1          | 6.25                                                         | 9.4  | 58          | 0.44      | 16.6                       | 0.19 | 89.4                        | 9.3  | On<br>1MV/m  |
| 5.8                                     | 347            | 1.9          | 95.9                                                         | 2.9  | 275         | 0         | 105.2                      | 1.1  | 23.1                        | 2.4  | Off<br>1MV/m |
| Reactive Switching Power <b>14576 W</b> |                |              | Reverse Voltage <b>384 V</b><br>Reactive Power <b>4400 W</b> |      |             |           | React. Power <b>1852 W</b> |      | React. Power <b>13303 W</b> |      | Max<br>4MV/m |


$$Z_{on} = 0.11 + j6.16 \quad Z_{off} = 0.1 - j10.65 \quad \delta F = \frac{V_{loop}^2}{8\pi W} \left[ \frac{1}{\text{Im } Z_{on}} - \frac{1}{\text{Im } Z_{off}} \right] = 230.6 \text{ Hz}$$

$$\text{Reactive Switching Power } P_{react} = 8\pi \delta F W E^2 = V_{loop}^2 E^2 \left[ \frac{1}{\text{Im } Z_{on}} - \frac{1}{\text{Im } Z_{off}} \right] = 14746 \text{ W.}$$

# Damper Assembly

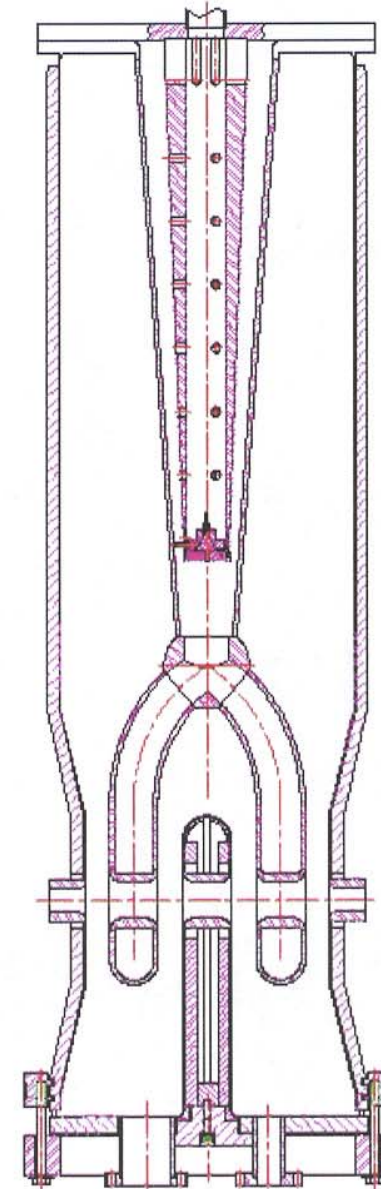



# Damper Details

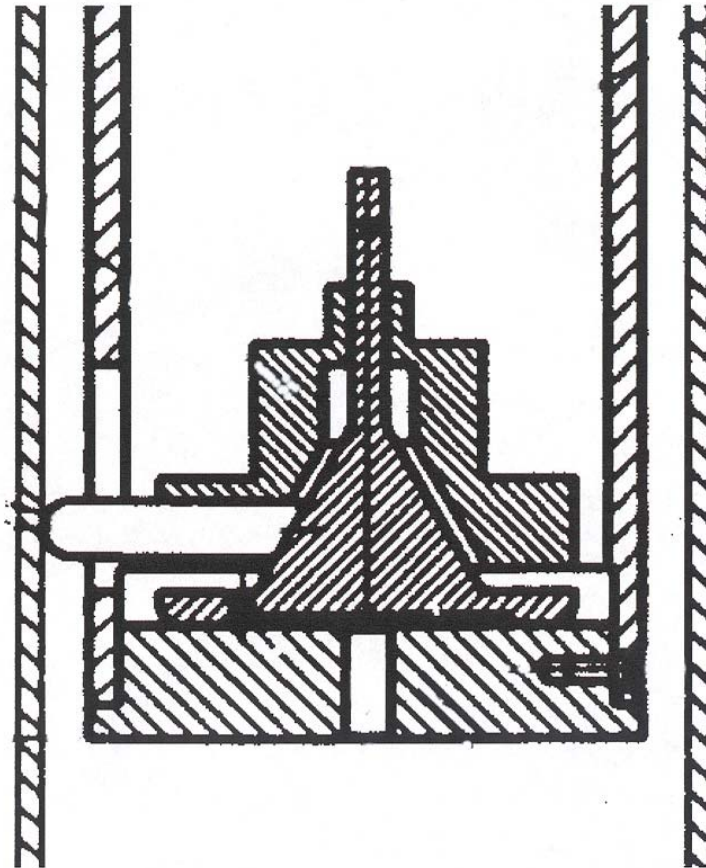
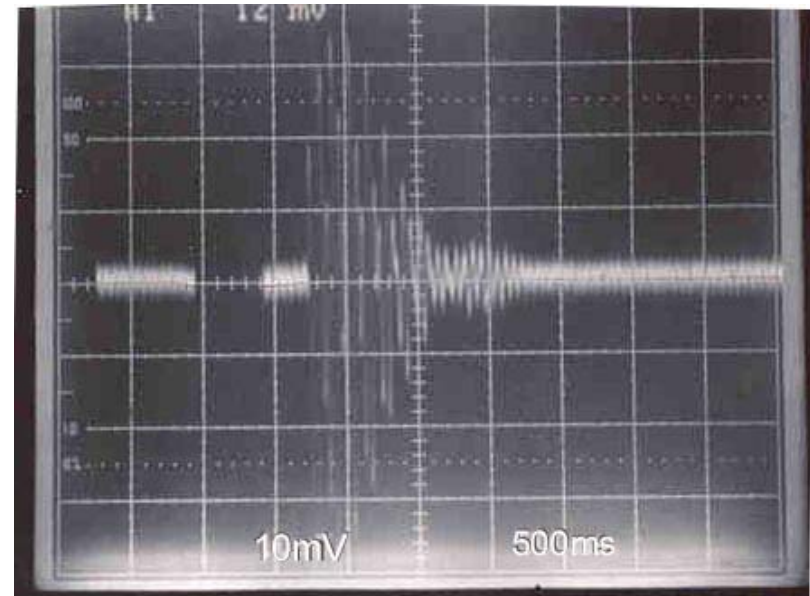
# Mechanical Damping Results


- Vibration decay time without damper = 28sec
- Vibration decay time with damper = .5sec



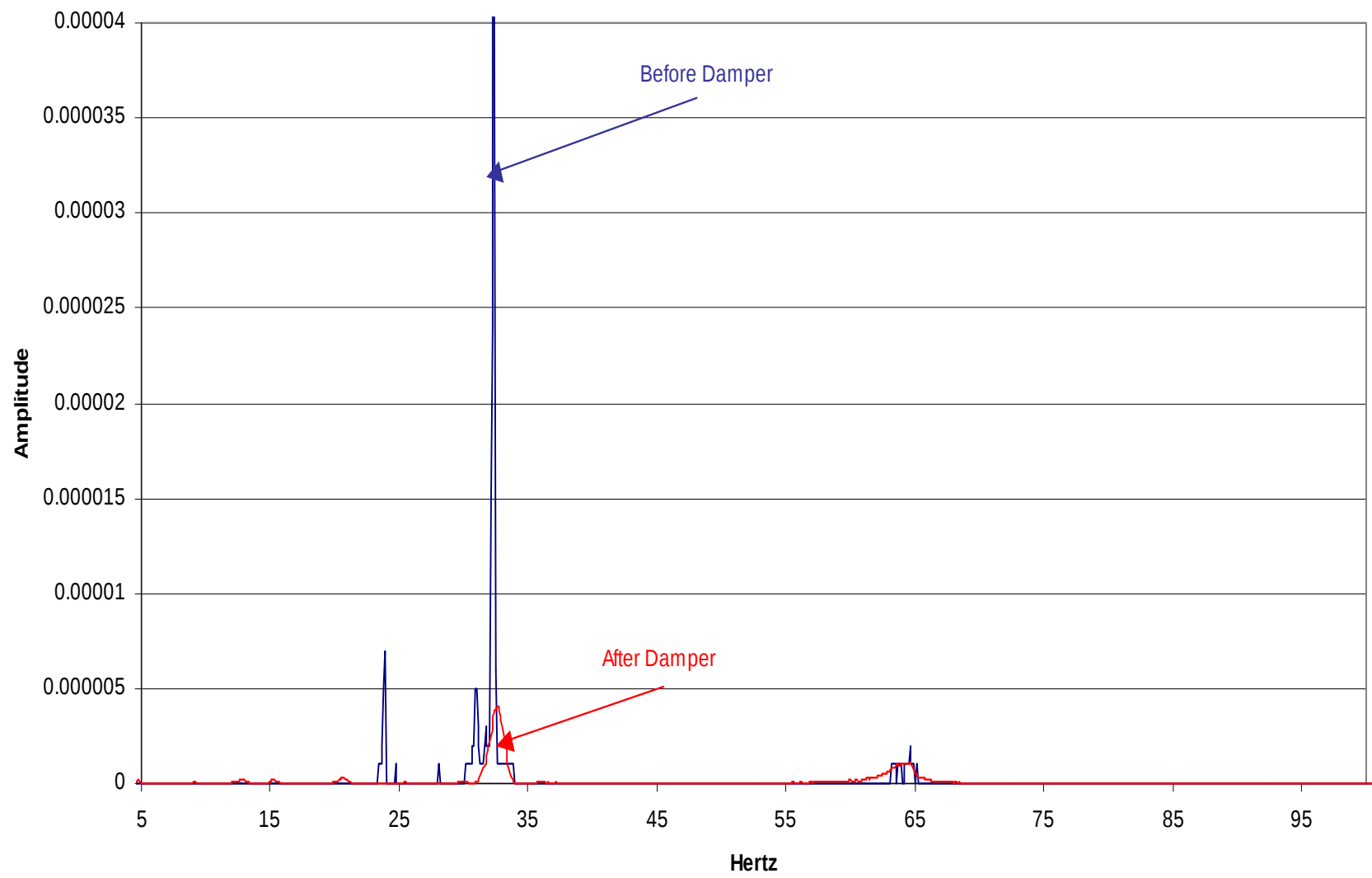



# Fast Tuner Mechanical Diagram

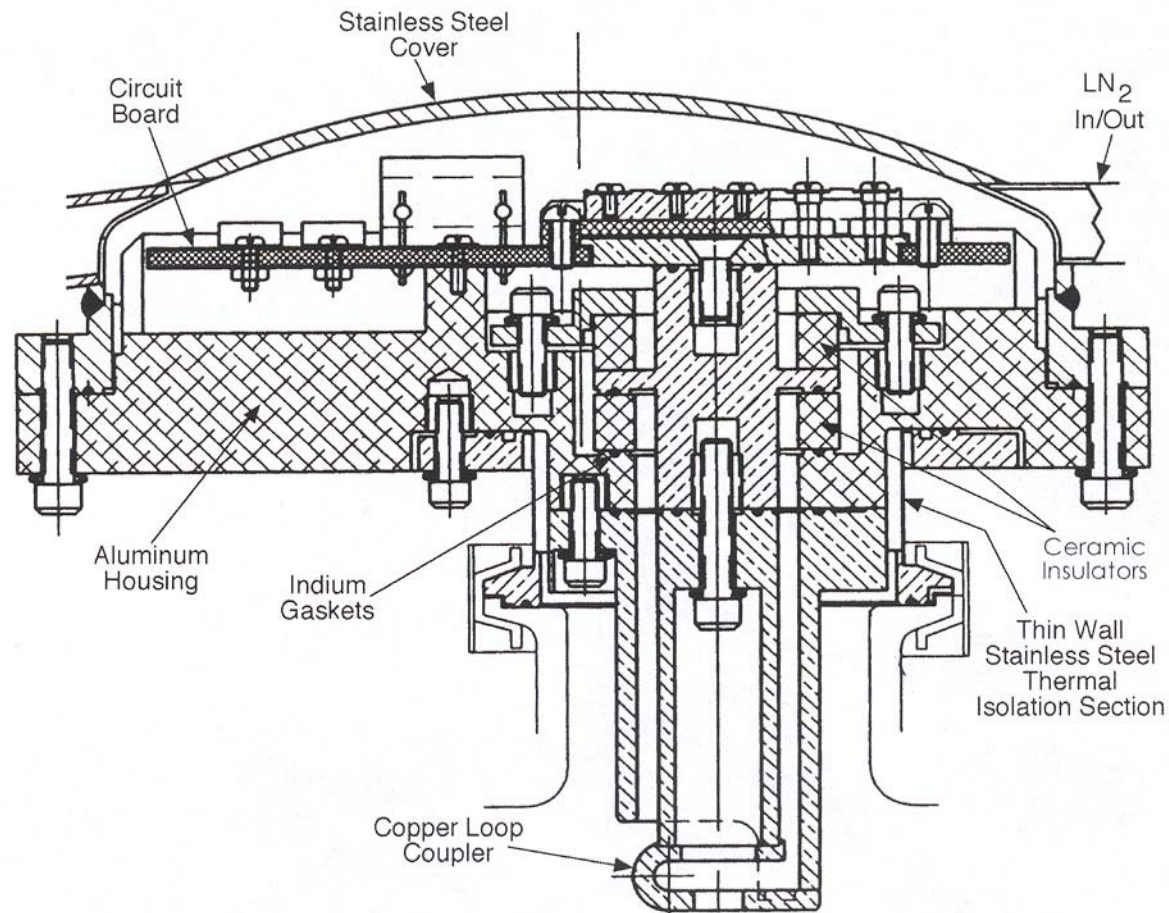

### PIN Diode Drive Requirements

- Square wave switching must occur at a fast enough rate that resonator phase wobble is acceptable.

$$\phi = 2\pi (F_{\text{window}})(1/2 \text{ switching period})$$

$$\phi = \left[ 2\pi \frac{\text{Radians}}{\text{Cycle}} \right] \left[ 250 \frac{\text{Cycles}}{\text{Second}} \right] (1/2) (4 \times 10^{-5} \text{ second})$$

$$\phi = 0.0314 \text{ radians} = 1.8 \text{ degrees}$$

|                                 |
|---------------------------------|
| Window = 250 Hz                 |
| Diode switching                 |
| Period = $4 \times 10^{-5}$ sec |
| 25 KHz                          |

This means that resonator phase deviation, per PIN diode switching cycle, can be as large as  $\pm 0.9$  degrees.


- PIN diodes must be driven to a sufficiently high reverse bias (OFF) that coupled resonator fields do not cause forward bias to occur. Typically, 675 volts of reverse bias is used.
- PIN diodes must be driven into sufficient forward bias (conduction) that coupled resonator fields do not remove the stored charge. (If forward bias is not sufficiently large, the diodes behave as lossy switches.) Approximately 2.0 amperes of forward bias current is used (9 diodes).
- Transitions of PIN diode bias must occur in 100 nanoseconds or less.  

This means      ON  $\rightarrow$  OFF  
                    and        OFF  $\rightarrow$  ON.

This requirement is necessary because, as the diodes switch states, a region of impedance is traversed where maximum RF energy is coupled into the VCX.


The region must be crossed as quickly as possible to avoid excessive RF energy dissipation.

# Switching Rise Time

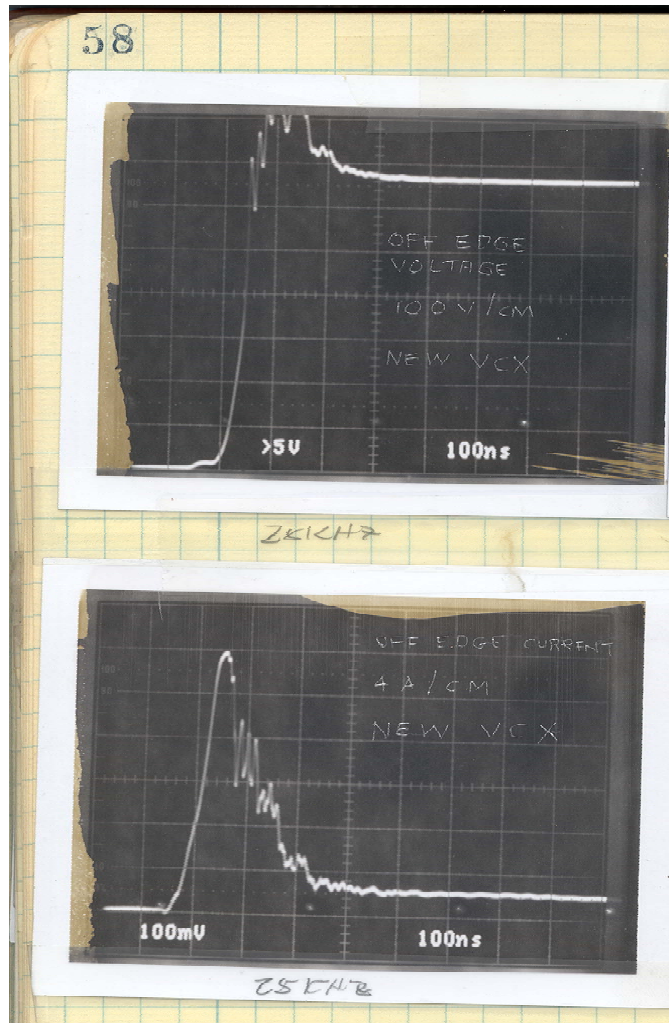

Off edge voltage  
100 V/cm  
~ 75 ns rise time

Off edge current  
4 A/cm

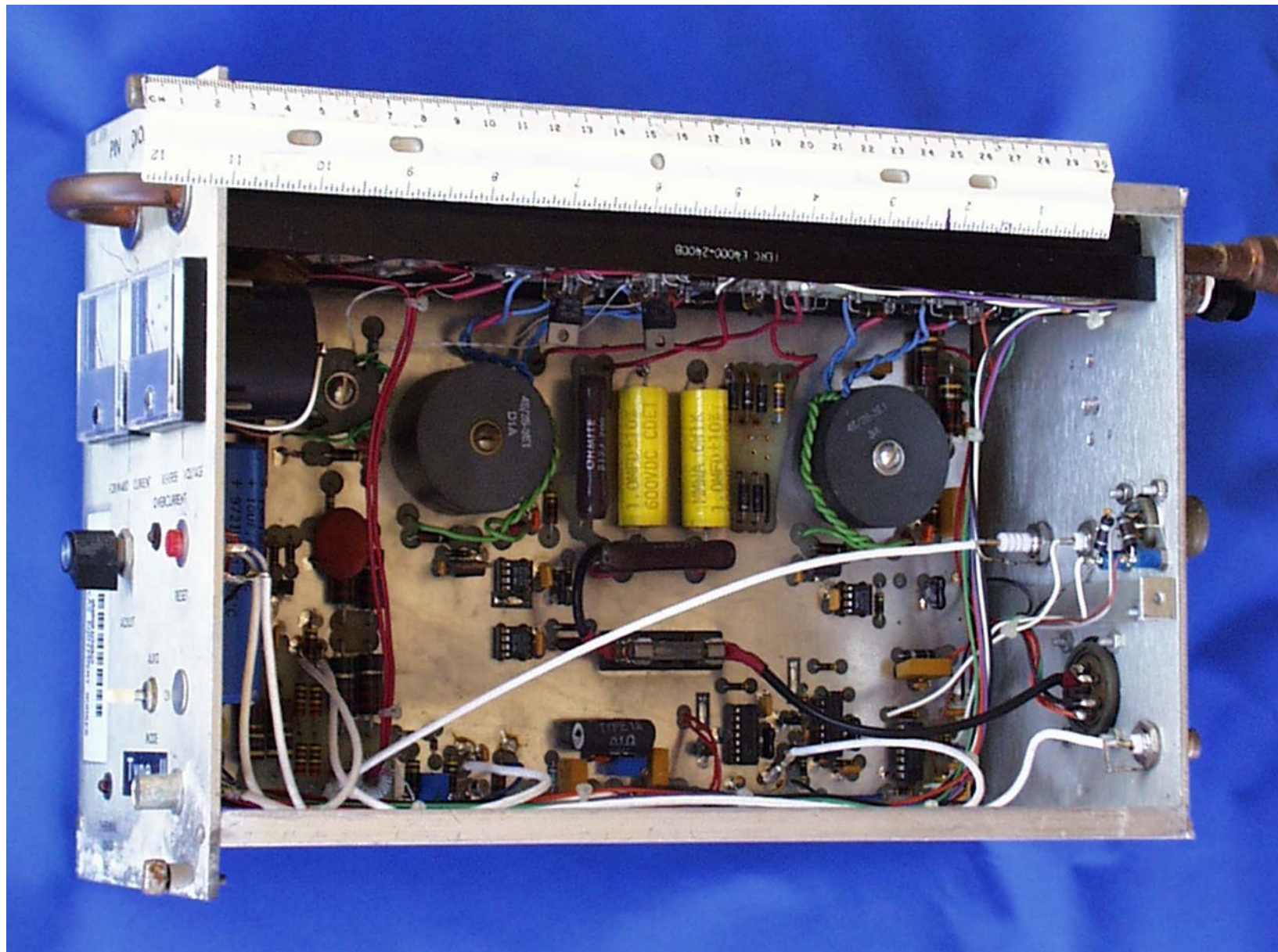

Workshop on Low-Level RF Controls For  
Superconducting Linacs

*ATLAS*  
*Argonne National Laboratory*

*G. P. Zinkann*

# Summary

|                                            |                    |
|--------------------------------------------|--------------------|
| Cavity Frequencies                         | 48.5 MHz to 97 MHz |
| Typical on-line windows                    | 200 to 500 Hz      |
| Max. Tested Reactive Power                 | 30KVA              |
| Measured heat load into resonator at 30KVA | 2 watts            |
| Typical PIN Diode Stored Charge            | 85nC               |
| Typical Diode Switching Losses             | 15 Watts           |
| Typical RF Loss into LN2                   | 150 to 200 Watts   |
| Total System Costs                         | \$7,000.00         |